
 

 
# 1 ADC / DAC

Petite puissance :  
Haute vitesse :  
Operational amplifier:



$$U_1 = -2I_q R_1 = -2R_1 \frac{U_D}{2r_s} = -\frac{1M\Omega}{2.5k\Omega} U_D = -400 \cdot U_D$$

$$U_2 = -S_2 U_1 R_2 = -5 \frac{mA}{V} \cdot 100k\Omega \cdot U_1 = -500 \cdot U_1$$

$$A_D = (-400) \cdot (-500) = 2 \cdot 10^5$$

$$f_0 = \frac{1}{2\pi R_1 C_k} \cdot \frac{r_{e5}}{R_2}$$

## ADC

**Quantization of the amplitude** Resolution N is the number of bits


Resolution step is the analog value of the interval between two codes (1LSB)

$$Code = \frac{V_{in}}{V_{FS}} \cdot (2^N - 1)$$

Quantification de l'erreur:


$$Power : E_N = \frac{1}{V_{LSB}} \int_{-q/2}^{q/2} V_{ERR}^2(V_{IN}) dV_{IN} = \frac{V_{LSB}^2}{12}$$

$$U_N = \frac{V_{LSB}}{\sqrt{12}}$$

 

INL (Integral non linearity): différence entre la valeur


actuelle et la valeur idéale

 

DNL : différence entre le step actuel et le step idéal

DNL  $\leq -1$  : non monotonic

DNL  $\leq +1$  : missing code

 

SNR(signal over noise power ratio):

$$SNR_{dB} = 10 \cdot \log\left(\frac{\text{signal power } P_S}{\text{noise power } P_N}\right)$$

$$SNR_{dB} = 20 \cdot \log\left(\frac{\text{signal RMS voltage } U_S}{\text{noise RMS voltage } U_N}\right)$$

THD (Total Harmonic distortion): ratio entre deux valeurs RMS

$$THD = \sqrt{\frac{U_{h2}^2 + U_{h3}^2 + \dots + U_{hn}^2}{U_{Sin}^2}}$$

(résultat entre 0 et 1)

SINAD (signal to noise and distortion):


$$SINAD = 10 \cdot \log\left(\frac{A_{SinFS}^2}{\sum(\text{noise} + \text{distortion}) \text{ power to } fs/2}\right)$$

(Effective number of bits):


$$ENOB = \frac{SINAD_{dB} - 1.76}{6.02}$$

Structure unary : série of  $2^N$  times  $2^0$  values

Resistor chain (kelvin divider)

 


Segmented chains:

 


Structure binary : N different values ( $2^0, 2^1, 2^2, 2^3 \dots 2^{N-1}$ )

Binary-weighted structure

 


U-I output:


Best AC performance Best DC performance

 


ADC structures :

 

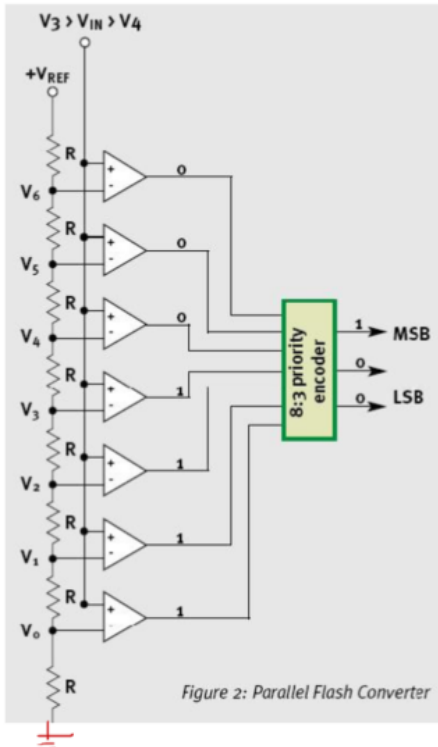
Flash converter:  $2^N$  resistors and  $2^N$  comparators. Speed between 100M and 1G sps. No S/H needed.



 Pipeline converter: chaque étage représente un bit. Speed between 1M and 500M sps. S/H needed at each stage.




 SAR converter: speed between 100k and 10M sps. Need S/H.



Noise sources:

 - quantization noise
- noise generated by the converter itself
- application circuit noise (reference & power supply, GND bounce, layout considerations)
- Clock jitter (sampling)



Analog input circuit noise is additive. Voltage reference noise is multiplicative. Quantisation noise is additive. Single ended and common mode:


 


Figure 6.11: Single-Ended Single-Supply DC-Coupled Level Shifter

 Single ended to differential (AC) conversion :



Single ended to differential (DC) conversion :

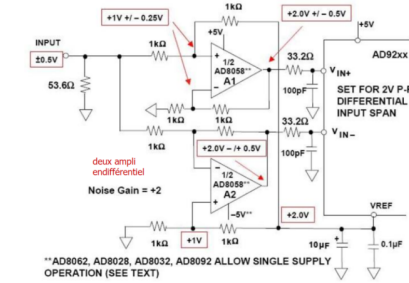


Figure 6.31: Op Amp Single-Ended to Differential DC-Coupled Driver with Level Shifting

## 1.1 Discrétisation

Valeur du signal continu pris à des temps précis (sample) Après l'échantillonnage, la valeur est quantifiée sur une valeur de  $2^n$

### 1.1.1 Idéal

$$x_s(t) = \sum_{k=-\infty}^{+\infty} x(kT_s) \cdot \delta(t - kT_s) = x(t) \cdot \sum_{k=-\infty}^{+\infty} \delta(t - kT_s) \quad (1)$$

### 1.1.2 Critère de Nyquist

$f_s > 2(f_a - f_b)$  avec  $f_a$  limite haute de la BW du signal et  $f_b$  limite basse de la BW

## 1.2 Aliasing

L'échantillonnage d'un signal provoque une répétition du spectre du signal autour de  $f_s$  et de multiples de  $f_s$ .

## 1.3 Signal Noise Ratio

- Bruit de quantification RMS  $N_{RMS} = \frac{V_{LSB}}{\sqrt{12}}$
- Tension sinus FullScale  $S_{RMS} = \frac{V_{LSB}}{\sqrt{2}} \cdot \frac{2^N}{2}$
- $SNR = 20 \log\left(\frac{S_{RMS}}{N_{RMS}}\right) = 20 \log\left(\sqrt{\frac{12}{8}}\right) + 20 \log(2^N)$
- En dB  $SNR = 6.02N + 1.76$

## 1.4 Process gain

C'est lorsque l'on utilise pas toute la bande de 0 à  $f_s/2$  le gain pour un sinus FullScale est le suivant.

$$SNR = 6.02N + 1.76 + 10\log\left(\frac{f_s}{2 \cdot BW}\right) \quad (2)$$


## 1.5 Sur-échantillonnage

$$SNR = 6.02N + 1.76 + 10\log(OSR) \quad (3)$$


Meilleur de 3dB à chaque fois que la  $f_s$  double.

## 1.6 Conversion Sigma-Delta


Modulateur de premier ordre

 

Analogique

 

Digital

 

Modulateur du deuxième ordre

### 1.6.1 Sur-échantillonnage pour SD

