


Contents

- Principles of DA and AD conversion
- Static performance characteristics of DAC and ADC
- Review of DA converter structures

- Exercices
- References

Converter's basics

⌘ Physical Domain ↔ Digital Domain

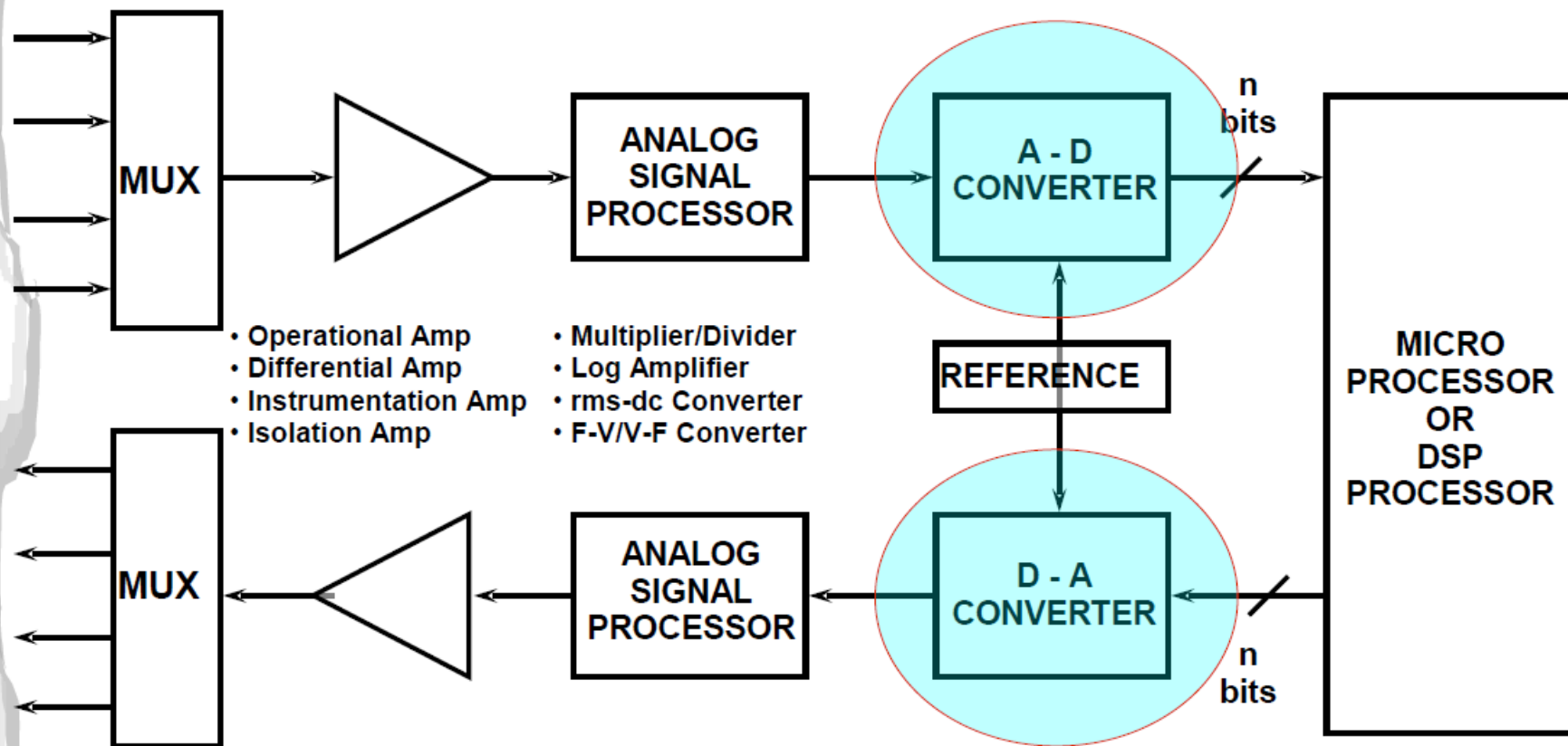

Converter's basics

AD & DA Converters are not only circuits but must be seen as a SYSTEM, with two kind of processes :

- ⌘ Quantization of the AMPLITUDE (today)
- ⌘ Quantization of the TIME (next week!)

AMPLITUDE Quantization

⌘ (Analog) Signal Vs (Digital) Number [1.2]

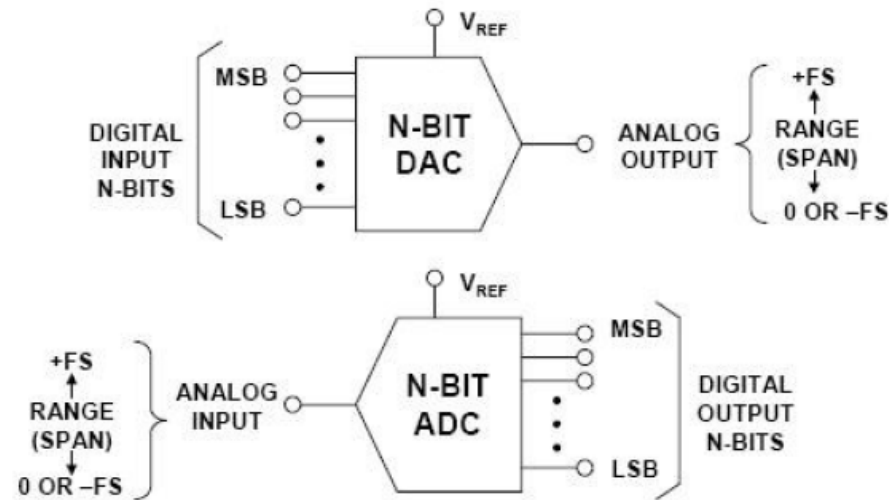


Figure 2.1: Digital-to-Analog Converter (DAC) and Analog-to-Digital Converter (ADC) Input and Output Definitions

Analog Side: Full Scale

- ⌘ Amplitude of the analog domain must meet the **Full Scale** of the converter (FS value)
 - FS is a technological constraint of the converter (Circuit selection!)
- ⌘ FS is related to a **Reference Value** (V_{REF})
- ⌘ « Input Voltage » right understanding!
 - Input Channel single-ended (SE) or differential (Diff) ?
 - Unipolar or bipolar ? Middle value of FS at 0V or $V_{CC}/2$ (or ...)

Analog Side: Dynamic Range

- ⌘ The Dynamic Range is the ratio of the larger and the smaller voltage of the INPUT SIGNAL
- ⌘ DR is a primary characteristic of the application, not of the converter!
- ⌘ Converter have to be better than signal's DR, but how much better?

Def. : Resolution

- ⌘ Resolution N is the *number of bits* of the digital number side
- ⌘ Resolution Step is the *analog value* of the interval between two adjacent code values, also called « 1 LSB »
- ⌘ 2^N digital levels (codes) : [0 to $2^N - 1$]
 - $\text{Nbr}_{\text{MAX}} = 2^N - 1$: « 1111111... »
 - By def. « all-1's code » \Rightarrow 1 lsb below FS value


Coding style of numbers

- ⌘ Number's coding : format of codes are ...
- Straight binary
 - (Gray)
 - Offset binary
 - 2's complement
 - (1's complement)
 - (sign + magnitude)

Def. : Transfer Function

⌘ Ideal TF

 
$$\text{Code} = \frac{V_{\text{IN}}}{V_{\text{FS}}} * 2^N - 1$$



Amplitude quantization error

⌘ Power :
$$E_N = \frac{1}{V_{\text{LSB}}} \int_{-q/2}^{q/2} V_{\text{ERR}}^2(V_{\text{IN}}) dV_{\text{IN}} = \frac{V_{\text{LSB}}^2}{12}$$
 
$$U_{N(\text{RMS})} = \frac{V_{\text{LSB}}}{\sqrt{12}}$$




Amplitude quantization error

- Quantization error is assumed to be white noise : folded in the base band, the noise level is $(1.76 + N \cdot 6.02) \text{ dB}$ below the full-scale SINUS power level.

=> quantization is distortion!

 (of synchronously sampled, periodic signals,
in all other cases, assimilate with white noise)



Real Transfer Function

⌘ Ideality don't exist in physics !

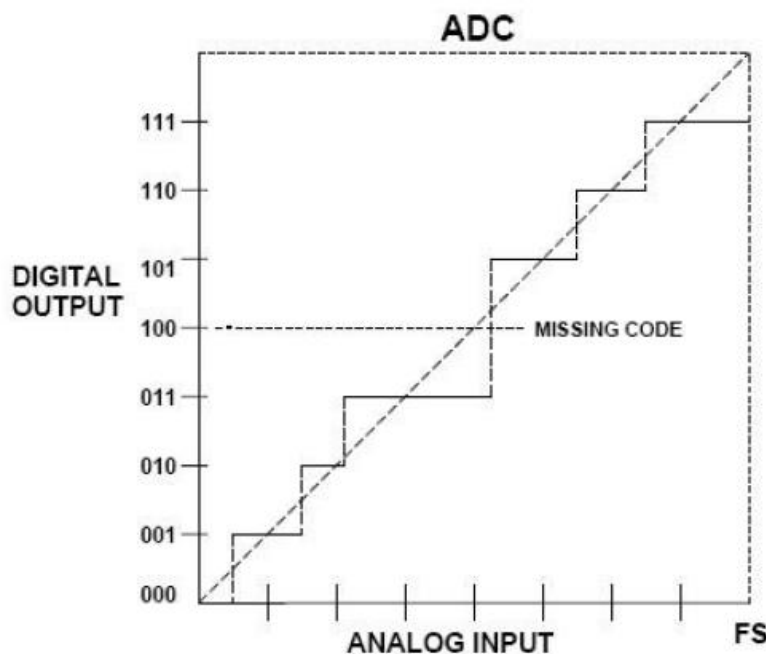
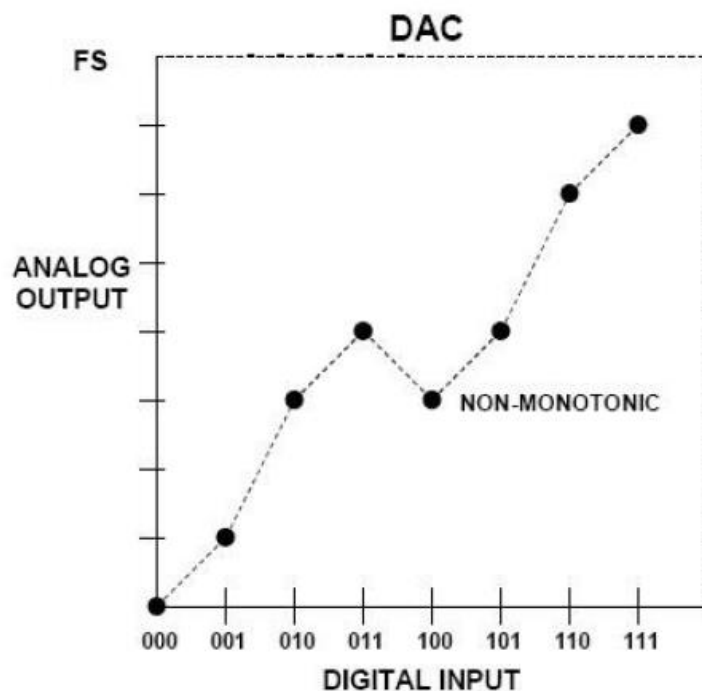


Figure 2.19: Transfer Functions for Non-Ideal 3-Bit DAC and ADC

Def. : INL


- ⌘ Integral Non-Linearity : a mesure of the distance of the current Transfer line Function to the ideal TF
- A static parameter
 - Measure on the analog side!
 - Unity : in #LSB or in %FS

DC ACCURACY					S, B versions, $V_{DD} = (2.35 \text{ V to } 3.6 \text{ V})^4$; A version, $V_{DD} = (2.7 \text{ V to } 3.6 \text{ V})$
Resolution	12	12	12	Bits	Guaranteed no missed codes to 12 bits
Integral Nonlinearity ³		±1.5	±1.5	LSB max	
	±1	±0.6	±0.6	LSB typ	
Differential Nonlinearity ³		-0.9/+1.5	-0.9/+1.5	LSB max	
	±0.75	±0.75	±0.75	LSB typ	
Offset Error ³		±1.5	±2	LSB max	
	±0.5			LSB typ	
Gain Error ³		±1.5	±2	LSB max	
	±0.5			LSB typ	

INL

⌘ INL values are « lower » as we choose a best fitting line !

- Zero-based line
- Best fitting line

 

INL

- ⌘ INL is the measure of the overall linearity (also called « precision »)
 - INL's profile is significative of the internal structure of the converter.
- ⌘ INL isn't allways needed! (feedback loop systems)
- ⌘

INL example

⌘ AD 7687, Analog Devices

 


Figure 1. Integral Nonlinearity vs. Code

Def. : DNL

⌘ Differential Non-Linearity : difference of each current step value of the TF from the ideal one

- Measure on the analog side
- Unity : in #LSB or in %FS

 



Figure 2.20: Details of DAC Differential Nonlinearity

DNL


- ⌘ $DNL > -1$: non-monotonic
- ⌘ $DNL > +1$: missing code
- ⌘ DNL is important for :
 - Closed loop systems
 - When small variations most significatives than big DC steps (video, graphics, sensors ...)

DNL example

 **Integral Non-Linearity (INL)
vs Output Code**



 **Differential Non-Linearity (DNL)
vs Output Code**




Def. : SNR

- ⌘ SNR : Signal over Noise POWER Ratio
- ⌘ SNR is one of the expression of the fundamental limitation of the converter
 - => the *SNR of the input signal* is the most useful specification for the choice of the converter's resolution
- ⌘ Unit : $\text{SNR}_{\text{dB}} = 10 \cdot \log \left(\frac{\text{signal Power } P_S}{\text{noise Power } P_N} \right)$
- ⌘ Or $\text{SNR}_{\text{dB}} = 20 \cdot \log \left(\frac{\text{signal RMS Voltage } U_S}{\text{noise RMS Voltage } U_N} \right)$

Harmonic distortion

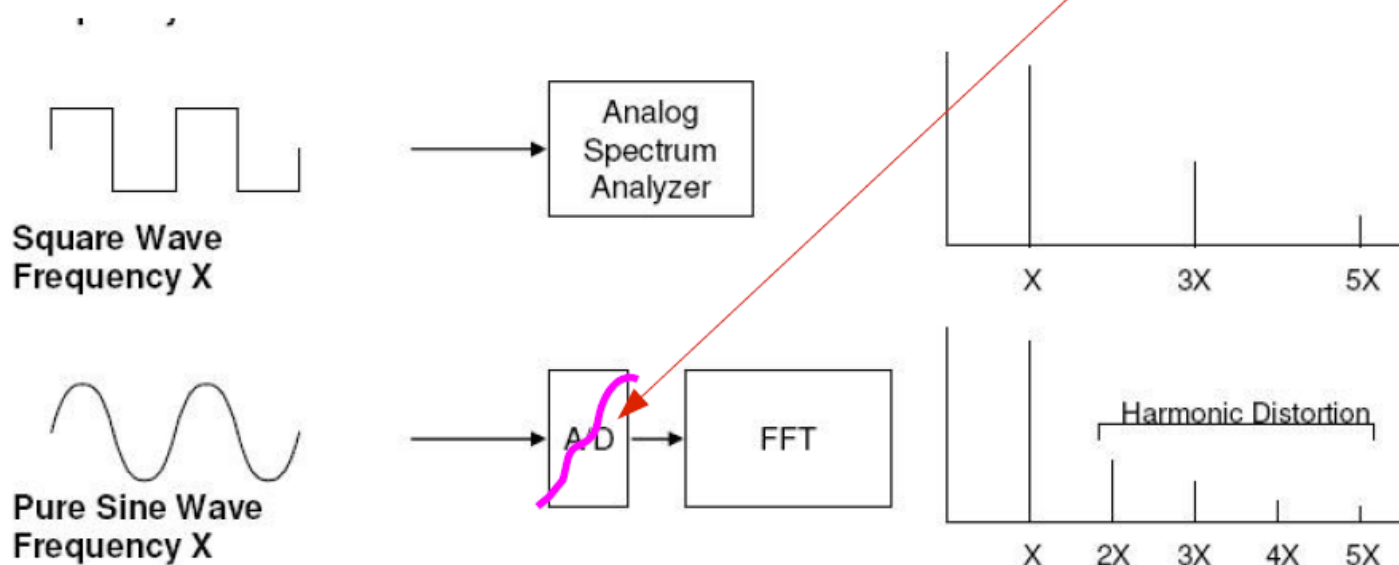- ⌘ 2nd order and 3rd order TF leads to distortion :
 - Pair and unpair harmonics are growing!
 - Distortion is a « dynamic » parameter but comes from the non-linearity of the TF



Total Harmonic Distortion THD

- ⌘ THD is the ratio of 2 RMS values :
- RMS value of the fundamental sinus
 - RMS value of a given number of harmonics

$$THD = \sqrt{\frac{\sum U_{h2}^2 + U_{h3}^2 + \dots + U_{hn}^2}{U_{sin}^2}}$$

Signal-to-Noise And Distortion SINAD

⌘ Distance between a sinus @FS amplitude and (noise + distortion) power is called SINAD

$$\text{SINAD} = 10 \log \frac{A_{\text{SinFS}}^2}{\sum (\text{noise} + \text{distortion}) \text{ power to fs/2}}$$

Effective Number Of Bits ENOB

⌘

$$\text{ENOB} = \frac{\text{SINAD}_{\text{dB}} - 1.76}{6.02}$$


⌘

ENOB says that the ADC is equivalent to this number of bits as far as SINAD is concerned

- That is, a converter with an ENOB of 7.0 has the same SINAD as a theoretically perfect 7-bit converter.

Spurious Free Dynamic Range SFDR

 ⌘ « Distance » to the highest distortion line



Data sheet analysis

Have a look at the following datasheets,

- DAC8411, MAX542
- AD7687, ADS5463

and determine the key performance characteristics: range, resolution, INL, DNL, SNR, THD, SINAD, ENOB, SFDR.

Exercise

DAC Structures


⌘ Unary and binary types

Unary: serie of 2^N times 2^0 (LSB) values

Next value always more: **monotonicity guaranteed.**




 Binary: N different values: $2^0, 2^1, 2^2, 2^3, 2^4 \dots 2^{N-1}$,
small in area, **MSB transition is critical:**



Unary Structures

 
- ✂ Simple D-A using a resistor chain (Kelvin Divider)



- Not practical for large N (2^N resistors!)
- Output is monotonic guaranteed


Unary Structures

⌘ Segmented chains

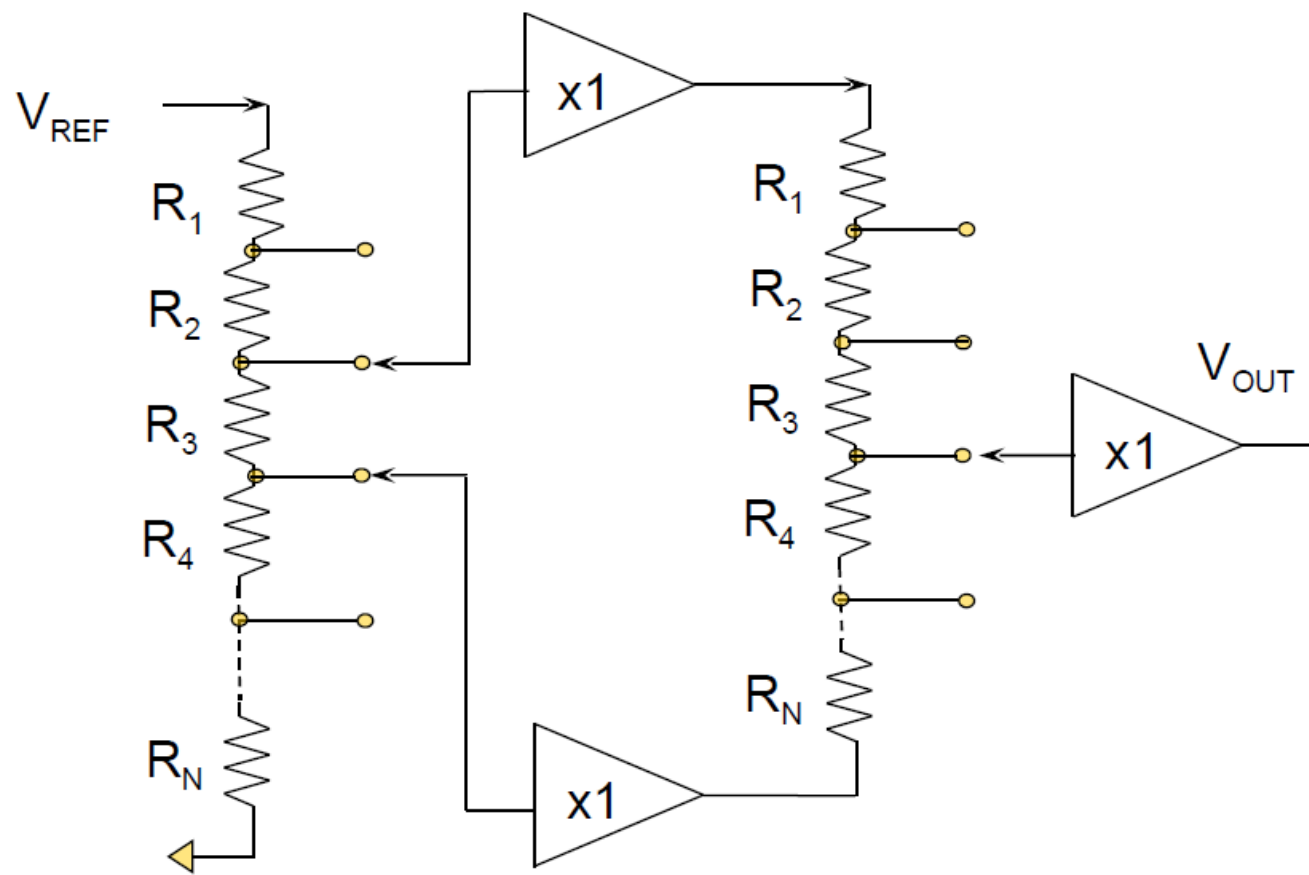

Binary-weighted Structure

⌘ A simple low-N U-DAC

 


- Matching of the current sources?

Binary weighted structure

The two schematics below show binary weighted structures for DA conversion. The principal inconvenients of the upper structure are

- The load of U_{ref} is not constant, but depends on z .
- The parasitic capacitances of the switches are (dis)charged when switching.

 
Explain why the lower schematic solves these problems.



Exercice

Binary-weighted Structure

⌘ A simple low-N U-DAC

 


- Matching easier! (only R & $2R$ values)
- Absolute Value Not Important (typ. 10-20k, +/- 20%)

Generalized ladder network

Draw a schematic of a voltage output 4bit-DAC with an R/2R ladder network, using commutators between two output current rails.

With the help of the circuit shown below, express R_l and R_p as functions of R_q , so that


$$U_2/U_1 = \alpha$$

 

 Exercice

Arrays of current sources

Instead of a reference voltage and a set of weighted resistors, a set of weighted current sources can be used for DA conversion as shown below.




Propose an alternative circuit using a set of current sources of same value and a ladder network for DA conversion.

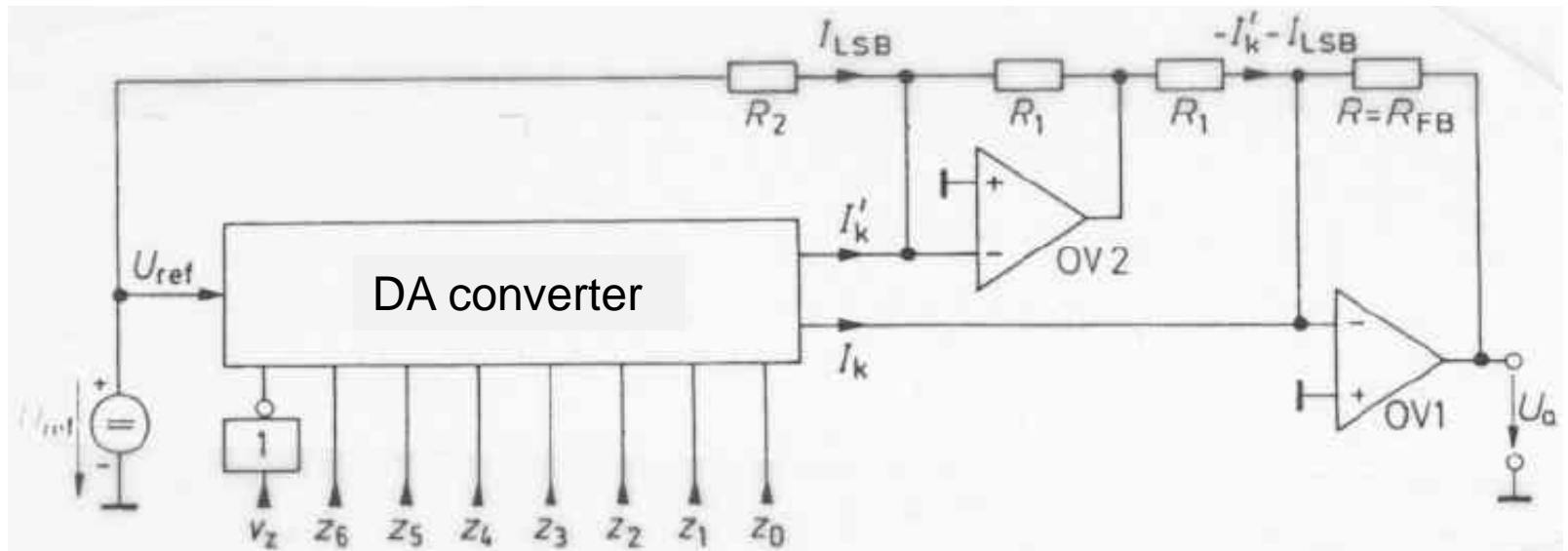Exercise

Bipolar output

For the circuit shown below, determine U_a as a function of Z , a signed binary number in 2's complement representation. I_k and I'_k are the two complementary current outputs of the DA converter.




What is the range of U_a ?

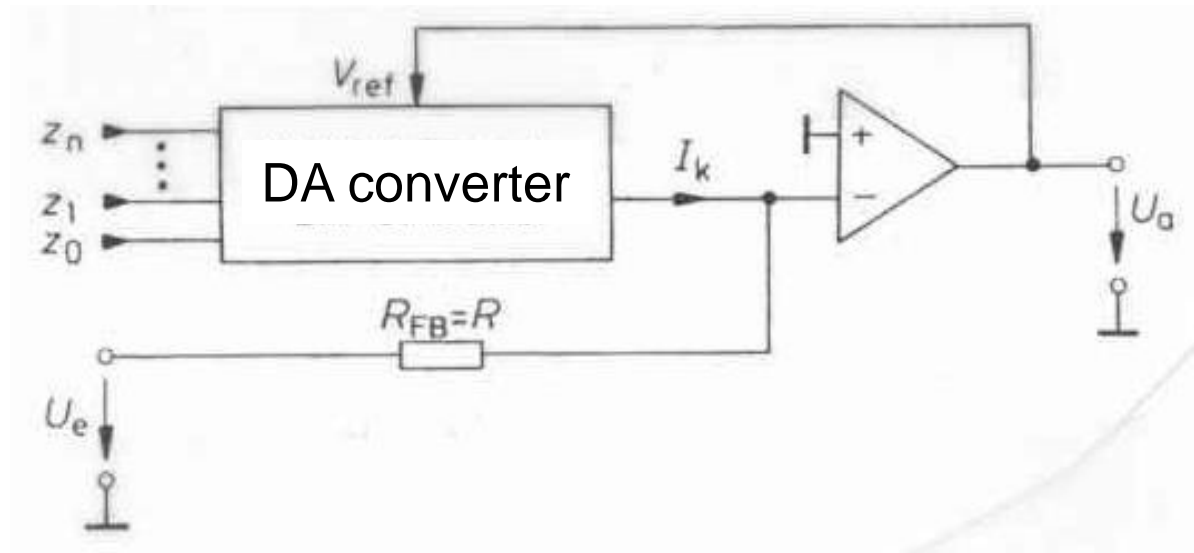Exercice

Multiplication / division

Show that in the circuit below, the output voltage U_a is proportional to U_e/Z .




Exercice


U-I output

- ✂ Use Voltage-output DAC for DC applications, Current-output for AC

Best AC performance

 

Best DC performance

 

Virtual Ground

DAC Summary

⌘ Unary (Resistor String)

- Inherent Monotonicity
- Compact Design Leading to the basis of Multi-Channel DACs
- Difficult to get High performance INL

⌘ Binary (R-2R Ladder)

- Good DC performance
- Suffer from distributed R-C effects and signal-dependant loading in frequency-domain applications
- Multiplying Capability
- Can Operate in Voltage Mode for Single Supply Applications

DAC Summary

⌘ Bipolar Switched Current

- Suffers AC limitations because R-2R is typically required to create LSB currents

⌘ CMOS Switched Current

- Best Choice for frequency-domain applications:
- No R-2R to limit AC performance
- Good matching for DC specifications (calibration sometimes needed)
- Allows for integration with discrete signal processing blocks to ease implementation and improve performance

References

W. Kester (ed.): *Analog-Digital Conversion*, Analog Devices 2004, ISBN 0-916550-27-3

This reference was used as a basis for the present presentation, a series of illustrations are taken from it.

The book is available for download on the moodle server.

Tietze, Schenk: *Halbleiter-Schaltungstechnik*, Springer 1999 (11th ed.), ISBN 3-540-64192-0